

Finite State Machine

AKHILA THALLA Roll No: FWC22312 akhilathalla0104@gmail.com

I. ABSTRACT

This paper explains a Finite State Machine by deconstructing the decade counter and here we verified the both incrementing decoder from 0 to 9 and decrementing decoder from 9 to 0 using arduino uno.

II. COMPONENTS

The required components list is given in Table: I., seven segment display is shown in Fig.1, and 7474 D-Flip Flop pin diagram is shown in Fig-2.

| Components | Value | Quantity |
|-----------------------|-------|----------|
| IC | 7474 | 2 |
| seven segment display | | 1 |
| Arduino | UNO | 1 |
| Jumper Wires | | 50 |
| Breadboard | | 1 |

TABLE I

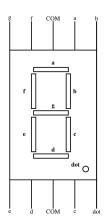


Fig. 1.



Fig. 2.

III. PROCEDURE

1) Make the connections of arduino, and two 7474 ICs according to Fig-4.

| | INPUT | | | | OUTPUT | | | | | | | | | |
|---------|-------|----|----|----|--------|----|----|----|--------------|------|----|---|----|----|
| | W | X | Y | Z | A | В | C | D | CLOCK D13 | | 5V | | | |
| Arduino | D6 | D7 | D8 | D9 | D2 | D3 | D4 | D5 | | | | | | |
| 7474 | 5 | 9 | | | 2 | 12 | | | CLK1 | CLK2 | 1 | 4 | 10 | 13 |
| 7474 | | | 5 | 9 | | | 2 | 12 | CLK1 | CLK2 | 1 | 4 | 10 | 13 |
| 7447 | | | | | 7 | 1 | 2 | 6 | | | | | 16 | |

Fig. 3.

2) Block diagram of fsm for decade counter

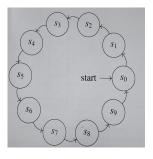


Fig. 4.

- 3) Block diagram of Decade Counter.
- 4) Block diagram of Decade Counter FSM implementation using D-Flip Flops.
- 5) Truth Table for incrementing from 0 to 9 in seven segment display

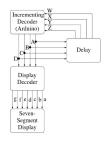


Fig. 5.

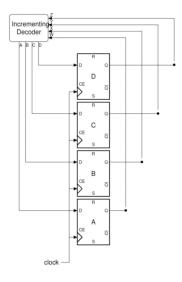


Fig. 6.

- 6) Truth Table for decrementing from $9\ {\rm to}\ 0$ in seven segment display
- 7) Execute the arduino code without any errors.
- 8) After upload the code into hardware setup using arduino IDE platform with hex file.

IV. RESULTS

- 1) Download the code given in the link below and execute them to see the output as shown in Fig.6,7.
- 2) https://github.com/Akhilathalla/Akhila/blob/main/fsm/main.cpp

| Z | Y | X | W | D | C | B | A |
|---|---|---|---|---|---|---|---|
| 0 | 0 | 0 | 0 | 0 | 0 | 0 | 1 |
| 0 | 0 | 0 | 1 | 0 | 0 | 1 | 0 |
| 0 | 0 | 1 | 0 | 0 | 0 | 1 | 1 |
| 0 | 0 | 1 | 1 | 0 | 1 | 0 | 0 |
| 0 | 1 | 0 | 0 | 0 | 1 | 0 | 1 |
| 0 | 1 | 0 | 1 | 0 | 1 | 1 | 0 |
| 0 | 1 | 1 | 0 | 0 | 1 | 1 | 1 |
| 0 | 1 | 1 | 1 | 1 | 0 | 0 | 0 |
| 1 | 0 | 0 | 0 | 1 | 0 | 0 | 1 |
| 1 | 0 | 0 | 1 | 0 | 0 | 0 | 0 |

TABLE II

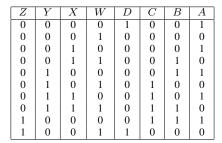


TABLE III

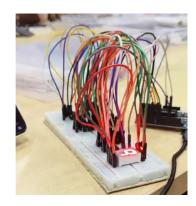


Fig. 7.

V. CONCLUSION

Hence implementation of 7474 IC Decade Couner on Seven segment dispaly using arduino UNO is done.